

This 51Ω resistor, R5, should be added *directly* between pins 2 and 4. Not doing so is one of the more common implementation errors with THAT Corporation's VCAs.

Theoretical considerations

Due to mismatches between certain internal components, both the 215x and 2181Lx VCAs require an external voltage divider network connected to pin 4. When properly adjusted, this divider network injects a voltage which compensates for the internal mismatches and minimizes the 2nd harmonic distortion that can otherwise result.

Figure 2 is taken from the THAT 2181x data sheet and shows a simplified internal schematic of the THAT 2181Lx VCA. One can see from this schematic that the base of lower logging transistor Q3 is cross-coupled to the base of upper anti-logging transistor Q2. Q1 and Q4 are similarly cross-coupled by way of a 27Ω resistor. When it comes to the 215x series, however, this connection is made *externally* (by R5, with a value of 51Ω).

In either case, the purpose of the resistor connecting the bases of Q1 and Q4 is to allow an external symmetry voltage to be applied to the base of Q4. This symmetry voltage, in turn, compensates for variations between the transistors of the gain cell, thereby minimizing 2nd harmonic distortion. In

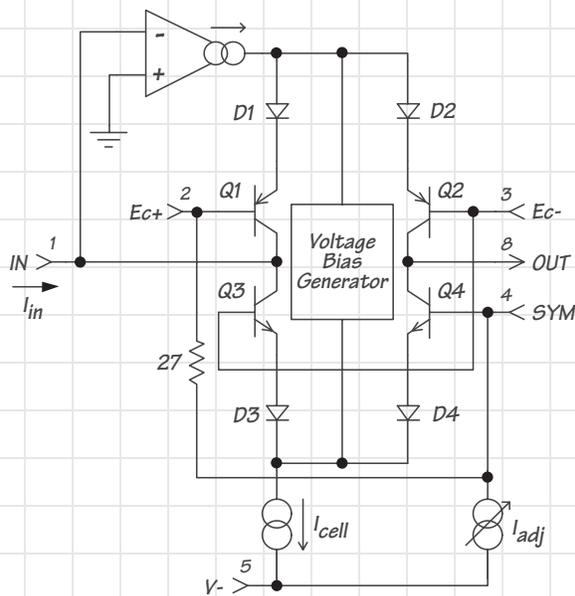


Figure 2: Simplified Internal Circuit Diagram

practice, pins 2 and 4 should never be more than a few millivolts apart.

In addition to reducing distortion, properly setting the symmetry voltage will minimize any DC offset changes ("thumps") that may occur with changes in gain.

As noted previously, when using the 215x series R5 should be connected *directly* between EC+ (pin 2) and SYM (pin 4), even when EC+ (pin 2) is grounded. This direct connection avoids any significant impedance between pin 2 and ground. Otherwise, any substantial ground currents (such as those which can occur when shield currents or relay drive currents are shunted through ground paths near the VCA) could result in error voltages developing at the control ports, resulting in a performance degradation. A good grounding scheme, of course, makes this concern superfluous, but we feel obligated to mention the issue since we have seen these mistakes in the past.

Summary

With very little effort, engineers can design their products to accept both the 2181Lx and 215x VCA series. Doing so provides some semblance of second sourcing, and helps ensure continued supply of VCAs even when one or the other series is in short supply.

VCA	C2	VR1	R4	R5
2151	47p	50 k Ω	470 k Ω	51 Ω
2150A	47p	50 k Ω	390 k Ω	51 Ω
2155	47p	50 k Ω	300 k Ω	51 Ω
2181LA	22p	50 k Ω	680 k Ω	-
2181LB	22p	50 k Ω	240 k Ω	-
2181LC	22p	50 k Ω	150 k Ω	-

Table 1: VCA specific component values